

Sequential circuits lecture notes

Note Title


Last time: Combinational circuits

- implement boolean fn of present inputs
- e.g. adder, decoder, multiplexer

Today: Sequential circuits

- implement boolean fn of present and past inputs
- typically use feedback to achieve this
i.e. one or more outputs "feed back"
as an input.

e.g.

 

Truth tables of sequential circuits can represent feedback either explicitly (in a separate column) or implicitly (use $Q(t)$ in output column)

inputs		outputs	
X	$Q(t)$	$Q(t+1)$	
0	0	0	<u>OR</u>
0	1	1	
1	0	1	
1	1	1	

X	$Q(t+1)$
0	$Q(t)$
1	1


We'll study several important sequential circuits:

- ① SR flip-flop (unlocked and clocked versions)
 - ② JK flip-flop
 - ③ D flip-flop
 - ④ read-write memory
 - ⑤ binary counter
- } clocked versions only

① (a) unclocked flip-flop

terminology: to set a bit means to assign it the value 1
to reset a bit means to assign it the value 0

 non-standard representation of S-R flip-flop:



exercise: when $R=1, Q=$
 $S=1, P=$
 $P=1, Q=$
 $Q=1, P=$

answers:

- 0
- 0
- 0
- 0


Thus have strange truth table:

inputs		outputs	
S	R	P	Q
0	0	1	0
0	1	0	1
1	0	1	0
1	1	0	1
1	1	0	0

} either is possible

If we agree that we'll never have S and $R = 1$ at the same time, we see from the truth table that

 $P = \bar{Q}$, so we can write the circuit as:



(this is the standard representation)


Exercise: fill in the sequence of outputs (this is not a truth table):

time t	S	R	Q	\bar{Q}
0	1	0	1	0
1	0	0	1	0
2	1	0	1	0
3	0	0	1	0
4	0	1	0	1
5	0	0	0	1
6	1	0	1	0
7	0	0	1	0

} answer

Note that $S \equiv$ "set" i.e. sets Q to 1
 $R \equiv$ "reset" i.e. resets Q to 0.

 circuit symbol for (unlocked) SR flip-flop:



①(b) Clocked SR flip-flop


A clock gives out a repeating on-off signal, e.g.

Attaching a clock to a circuit can make it change state exactly once per cycle e.g.

- when clock is 1
 - when clock is 0
 - when clock changes 0 → 1
 - when clock changes 1 → 0
- } level-triggered
- } edge-triggered

We don't study details of how this is achieved.

Symbol for clocked SR flip-flop:

 


Exercise: fill in the truth table on the handout (puzzle 1).

Briefer truth table:


S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	undefined

(2) JK flip-flop

circuit:

 

symbol:

 

truth table: same as SR, but output is toggled when $\overline{J+K}$ are 1:

\overline{J}	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\overline{Q(t)}$


Important lesson from toggling behavior:

At each clock tick, all flip flops compute output based on current input — but this output does not feed back and affect the inputs until the next clock tick.


Exercise: Understand this using above circuit diagram for JK flip-flop.

(4) D flip flop

circuit:

 

Symbol:

 


truth table:

D	Q(t+1)
0	0
1	1

Seems pointless, since $Q \equiv D$. Wouldn't a wire achieve the same thing?

Answer: No - it's all about timing. Q stays at a stable level between clock pulses. Meanwhile, we can adjust D.

 This leads to circuit for a 1-bit memory:



⑤ Read-writes memory

See textbook fig 3.32

Activity: do handout puzzles 2 and 3

⑥ Binary counter

See textbook fig 3.31

Activity: do handout puzzle 4.

If time, check out the online demo on resume page.